

# Lab 6: Negative Resistance

Ruby Spring

October 24, 2013

## Abstract

In this lab we built a 'negative resistor' and proved that it behaved as such by plotting voltage versus current and observing that current and voltage have an inverse relationship in said plot.

## 1 The Circuit

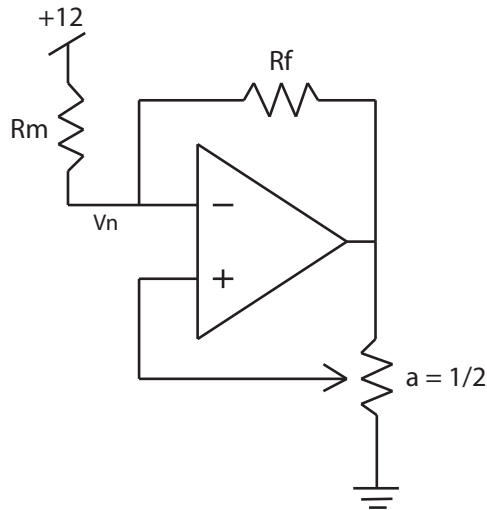


Figure 1: Circuit Diagram of negative resistor in series with  $R_m$

### 1.1 quantitative analysis

In order to prove that the resistance is 'negative', the configuration of the op-amp in fig.1 must be analyzed for  $V_n$  where  $a = \frac{1}{2}$ .

First we must write  $V_-$ ,  $V_+$ , and  $V_o$  in terms of our variables:

$$V_o = V_n - R_f i_n \quad (1)$$

$$V_- = V_n \quad (2)$$

$$V_+ = a V_o = a (V_n - R_f i_n) \quad (3)$$

$$(4)$$

For section I:

We assume...

$$V_+ = V_- \quad (5)$$

$$a(V_n - R_f i_n) = V_n \quad (6)$$

$$R_f i_n = \frac{aV_n - V_n}{a} \quad (7)$$

$$R_f i_n = V_n \frac{a-1}{a} \quad (8)$$

$$V_n = \frac{-a}{1-a} R_f i_n \quad (9)$$

$$V_n = -R_f i_n \quad (10)$$

...when

$$-V_s < V_o < V_s \quad (11)$$

$$-V_s < V_n - R_f i_n < V_s \quad (12)$$

$$-V_s + R_f i_n < V_n < V_s + R_f i_n \quad (13)$$

$$-V_s + R_f V_n * \frac{a-1}{aR_f} < V_n < V_s + R_f V_n \frac{a-1}{aR_f} \quad (14)$$

$$-V_s - \frac{1-a}{a} V_n < V_n < V_s - \frac{1-a}{a} V_n \quad (15)$$

$$-aV_s < V_n < aV_s \quad (16)$$

$$-6 < V_n < 6 \quad (17)$$

$$(18)$$

For section II:

When...

$$V_o = V_s \quad (19)$$

$$V_s = V_n - R_f i_n \quad (20)$$

$$i_n = \frac{V_s - V_n}{R_f} \quad (21)$$

or solving for  $V_n$ , which will be useful later:

$$V_n = V_s + R_f i_n \quad (22)$$

...we assume

$$V_+ > V_- \quad (23)$$

$$a(V_n - i_n R_f) > V_n \quad (24)$$

$$V_n > \frac{-a}{1-a} R_f i_n \quad (25)$$

$$\text{but we know from line 22 } V_n = V_s + R_f i_n \quad (26)$$

$$V_s + R_f i_n > \frac{-a}{1-a} R_f i_n \quad (27)$$

$$\frac{1-a}{1-a} R_f i_n + \frac{a}{1-a} R_f i_n > -V_s \quad (28)$$

$$\frac{R_f i_n}{1-a} > -V_s \quad (29)$$

$$i_n > \frac{a-1}{R_f} V_s \quad (30)$$

$$i_n > \frac{-6}{R_f} \quad (31)$$

$$(32)$$

For section III:

We can just borrow from section II and flip the signs:

We assume...

$$V_+ < V_- \quad (33)$$

$$i_n < \frac{6}{R_f} \quad (34)$$

...when

$$V_o = -V_s \quad (35)$$

$$i_n = \frac{V_n + V_s}{R_f} \quad (36)$$

or

$$V_n = R_f i_n - V_s \quad (37)$$

$$(38)$$

## 2 Results

Now we need to make use of the quantitative analysis. We can plot a theoretical graph of  $V_n$  versus  $i_n$  and plot experimental points over the graph to compare the two. The results are in fig. 2 below.

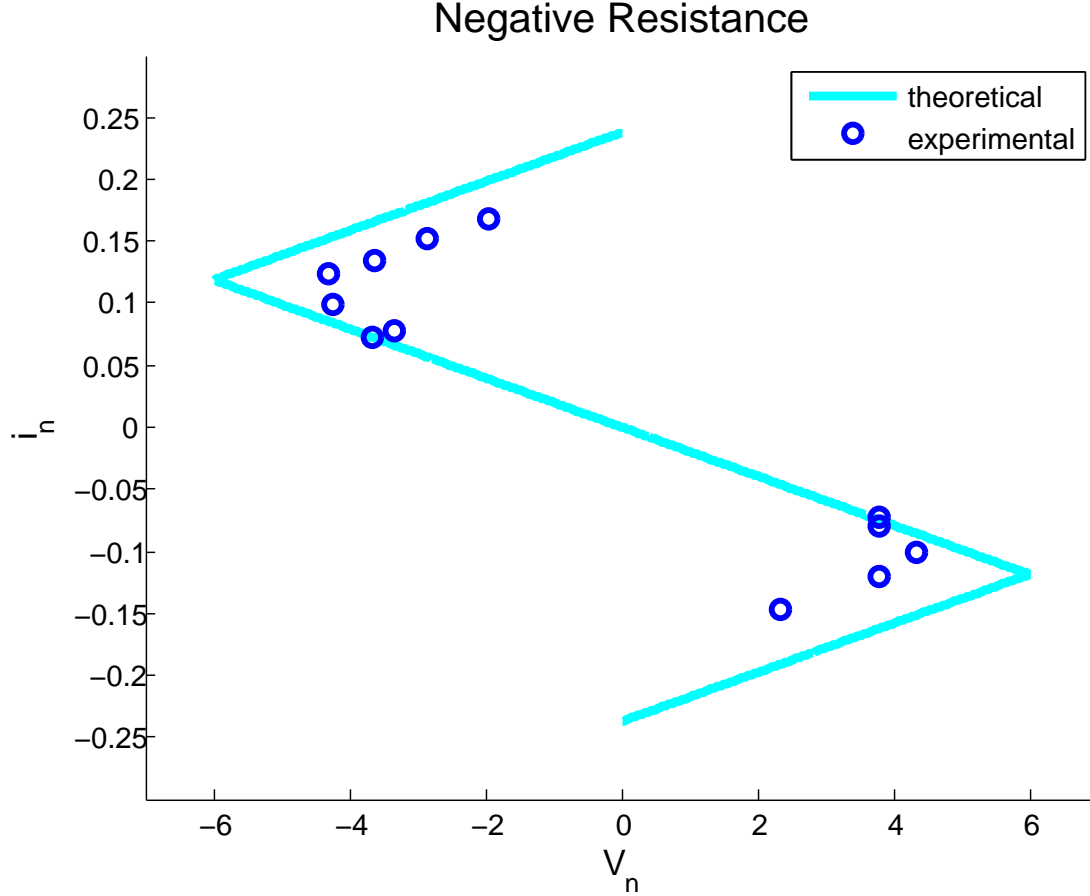


Figure 2: negative resistance graph

## 3 Qualitative Analysis

As you can see, the experimental data comes pretty close to theoretical in region I on the interval  $-4 < V_n < 4$ , and the slopes in regions II and III look accurate. But the op-amp was obviously not able to output enough voltage. Indeed, OPA's rails only reach about plus or minus 10 Volts as apposed to a theoretical plus or minus 12 Volts. This explains why the data 'falls short' of the theoretical.

### 3.1 A brief explanasion of the methods used to collect and implement the data

Strategic values of  $R_m$  were applied to the circuit and the resulting values of  $V_n$  were recorded. The current  $i_n$  was then found by using the equations  $i_n = \frac{V_s - V_n}{R_m}$  when  $V_s = 12$  and  $i_n = \frac{V_s + V_n}{R_m}$  when  $V_s = -12$ .