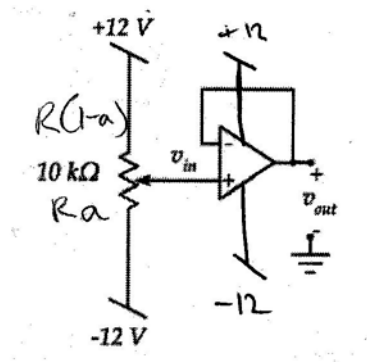


Lab 2

In this lab we used an Op-Amp for three circuits: a voltage buffer, a Schmitt trigger, and an inverted amplifier. We then graphed data for V_{in} vs. V_{out} from each circuit using a matlab program that pulls the data from a scope.

1. Buffer



This circuit provides variable input V_{in} and produces V_{out} equal to V_{in}

to find v_{out} :

$$V_{in} = V_s - \Delta V$$

$$\Delta V = I \cdot R(1 - a)$$

$$I = 2V_s / R$$

$$\Delta V = (2V_s / R) \cdot R(1 - a)$$

$$\text{therefore } V_{in} = V_s - 2V_s \cdot (1 - a)$$

$$\text{but } V_{in} = V_{out}$$

$$\text{Therefore } V_{out} = V_s - 2V_s \cdot (1 - a)$$



This is true for region I of the graph of V_{in} vs. V_{out}

$$\text{I. } V_{out} = V_{in} \text{ when } -V_s < V_{out} < V_s$$

$$\text{II. } V_{out} = V_s \text{ when } V_{in} > V_s$$


$$\text{III. } V_{out} = -V_s \text{ when } V_{in} < -V_s$$

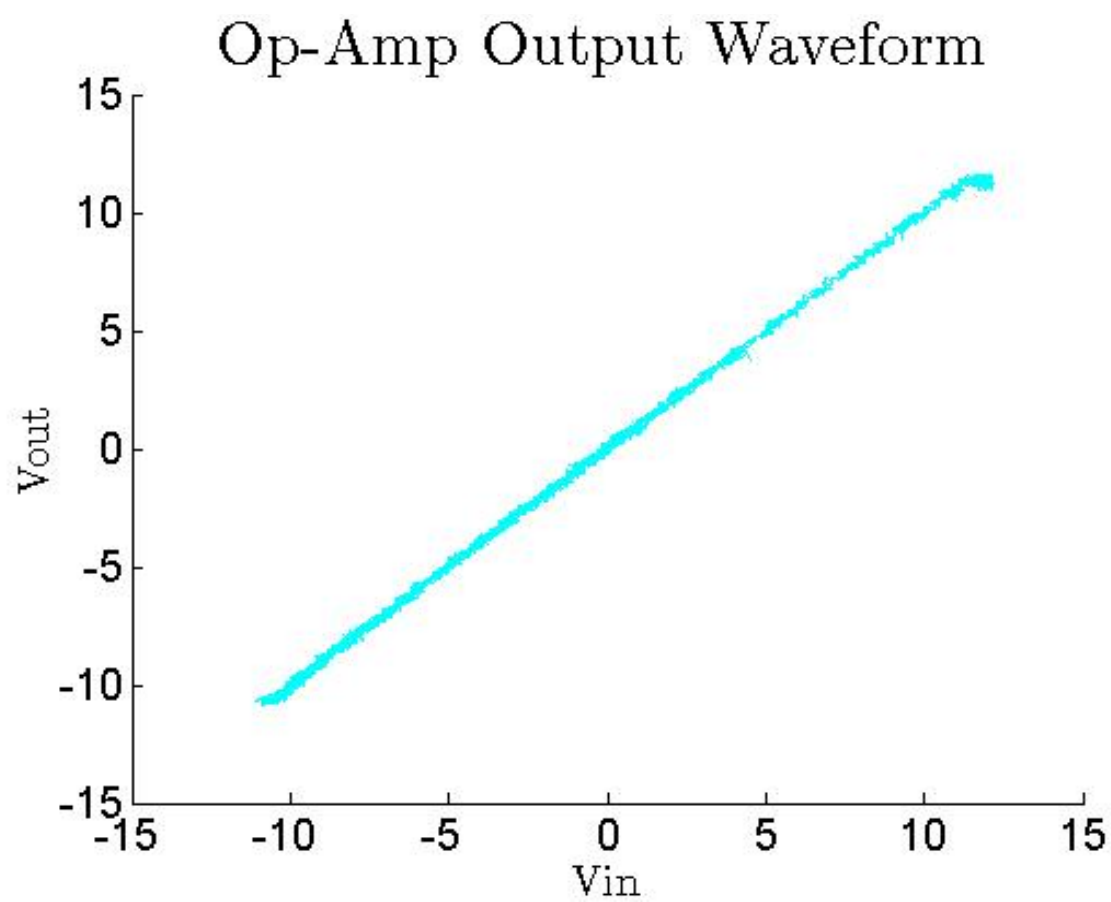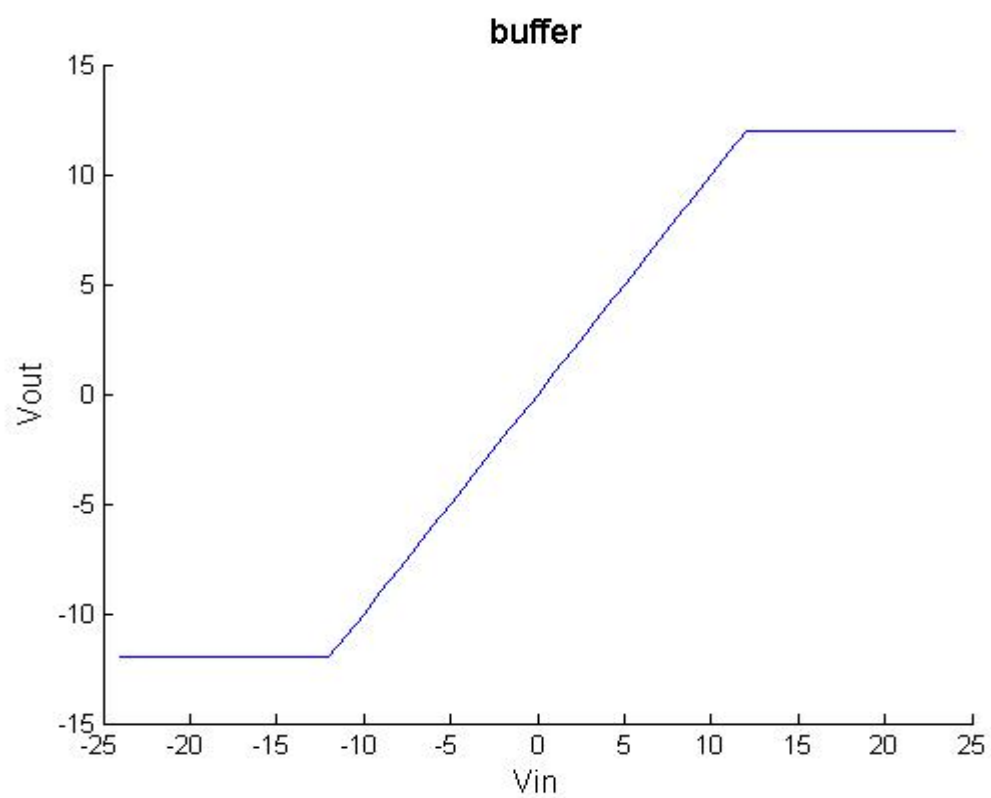Below is the theoretical graph followed by experimental data from the buffer.



2. Comparing two circuits

circuit 1:

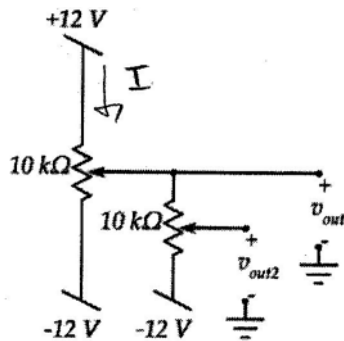

$$V_{out} = V_s - \Delta V$$


$$\Delta V = I \cdot R_{across V_{out}} = (2V_s / R_{eq}) \cdot (R/2)$$

$$R_{eq} = .5R \cdot R / (.5R + R) + R = 5R/6$$

$$V_{out} = V_s - (2V_s / (5R/6)) \cdot (R/2) = V_s - 12V_s/10$$

$$V_{out} = -2.4V$$

circuit 2 :

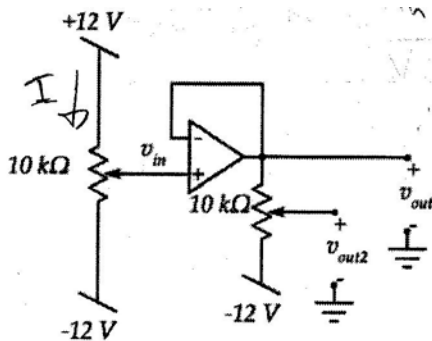


$$V_{in} = V_{out}$$

$$V_{in} = V_s - \Delta V = V_s - (2V_s / R) \cdot (R/2) = V_s - V_s = 0$$

$$V_{out} = 0$$

3. Schmitt Trigger

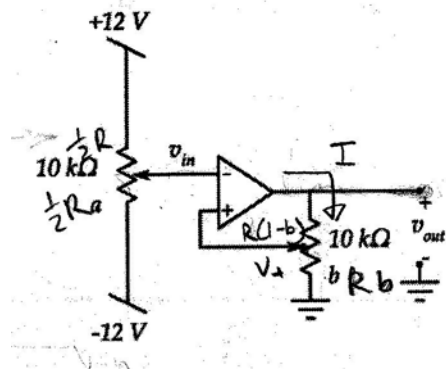

we know that for region I $V_{in} = V_- = V_+$ but what is V_{out} in terms of V_{in} ?

since $V_{in} = V_+$ and V_+ intersects with V_{out} , it will be helpful to find V_+

$$V_+ = V_{out} - I \cdot R(1-b)$$

$$I = V_{out}/R$$

$$\text{therefore } V_+ = V_{out} - (V_{out}/R) \cdot R(1-b)$$

$$\text{which simplifies to } V_+ = b \cdot V_{out}$$

$$\text{but we also know that } V_{in} = V_+$$

$$\text{therefore } V_{in} = b \cdot V_{out} \text{ and we can see that our slope for region I will be } 1/b$$


yay! now we know what our regions will look like:



$$\text{I. } V_{in} = V_- = V_+ \text{ and } V_{in} = b \cdot V_{out}$$

$$\text{II. } V_{in} < b \cdot V_{out} \text{ and } V_{out} = V_s$$


$$\text{III. } V_{in} > b \cdot V_{out} \text{ and } V_{out} = -V_s$$


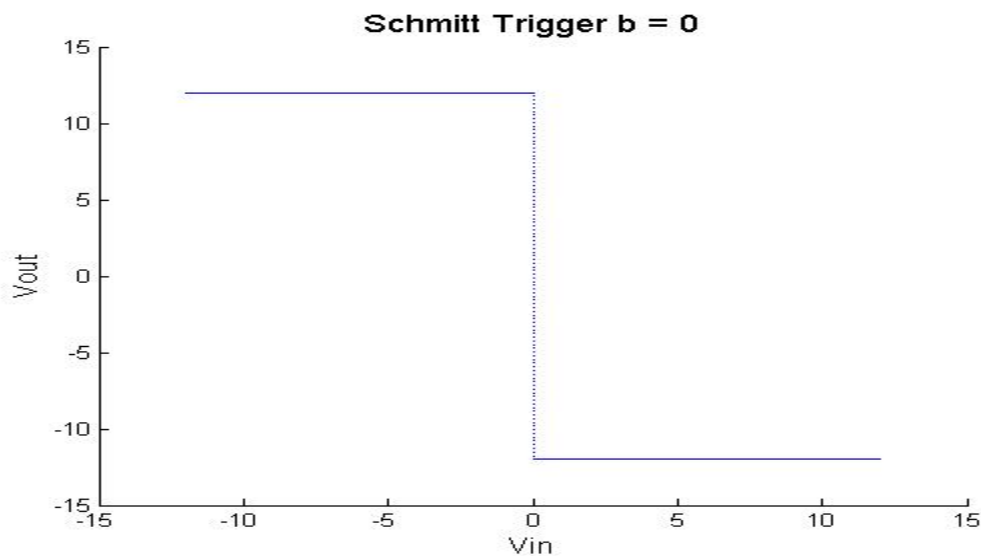
here are the theoretical graphs for three values of potentiometer b:



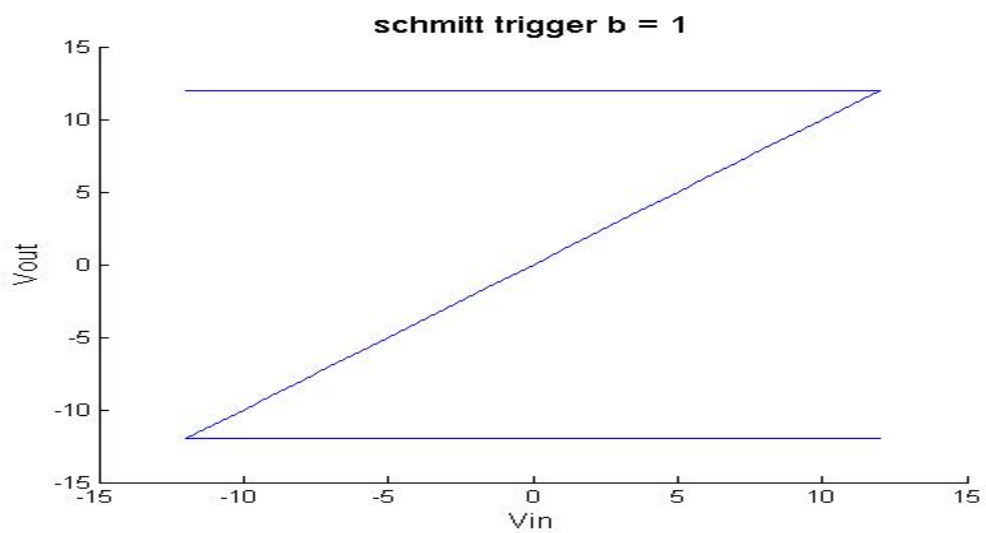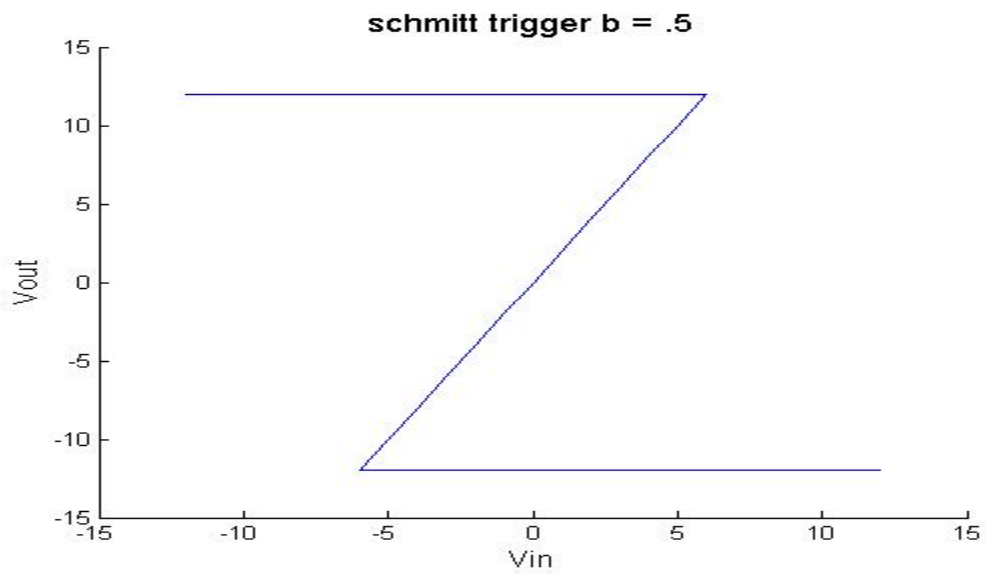


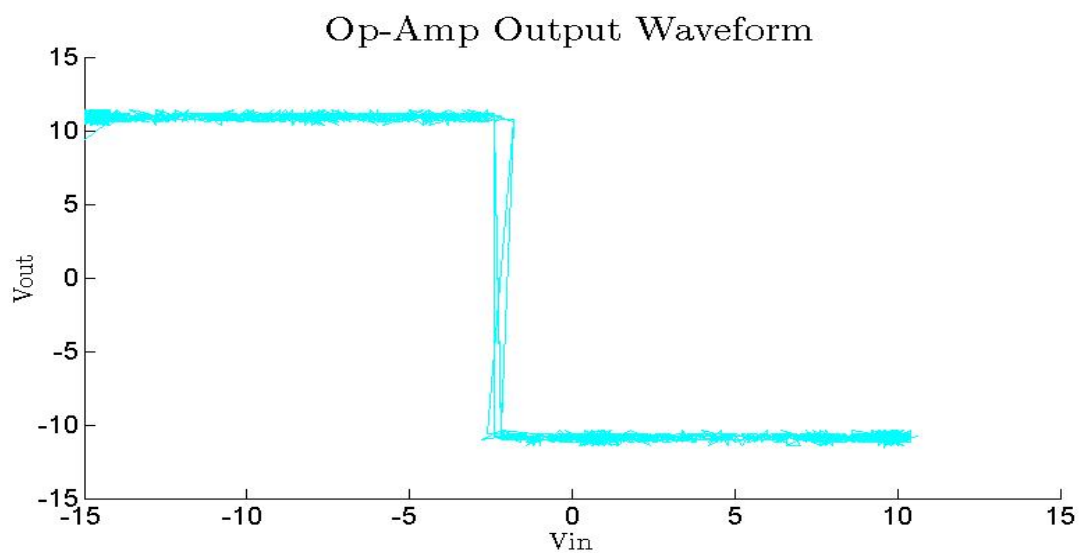here is the experimental data for three values of pot b! Any weird noise is probably a result of bad Op-Amp function.



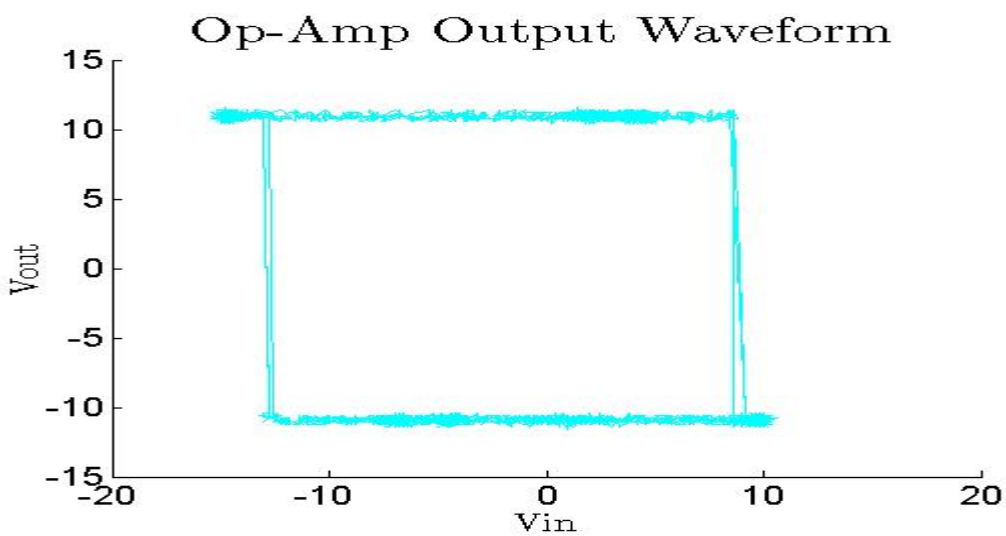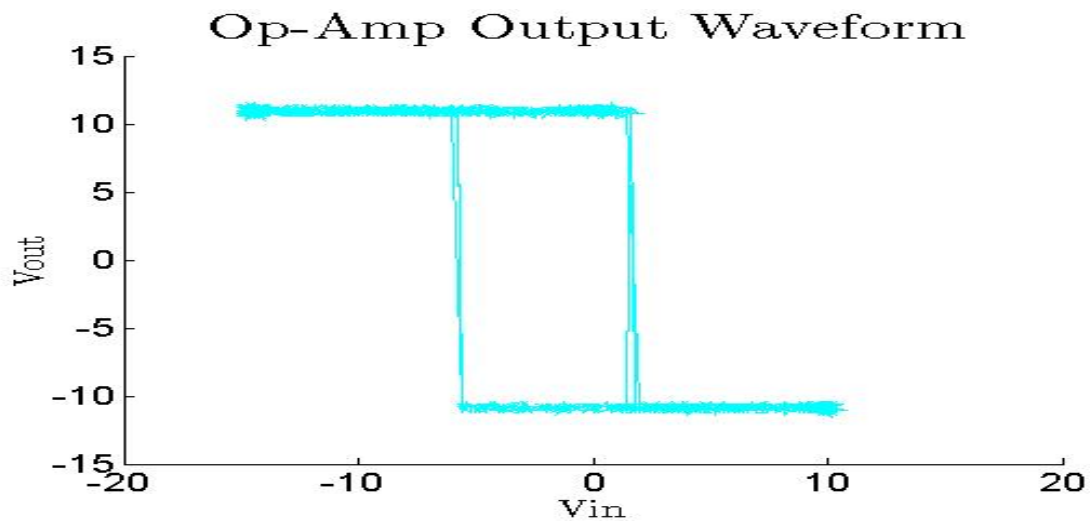

4. non-inverting trigger

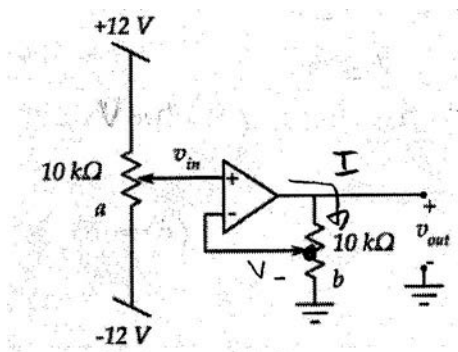

This circuit is the same as a shmitt trigger but with positive feedback instead of negative (aka positive and negative are swapped).

so all we have to do for region I is replace V_+ with V_- !



therefore $V_{in} = V_- = b \cdot V_{out}$ and for the three regions we have


I. $V_{in} = V_- = V_+$ and $V_{in} = b \cdot V_{out}$

II. $V_{in} > b \cdot V_{out}$ and $V_{out} = V_s$

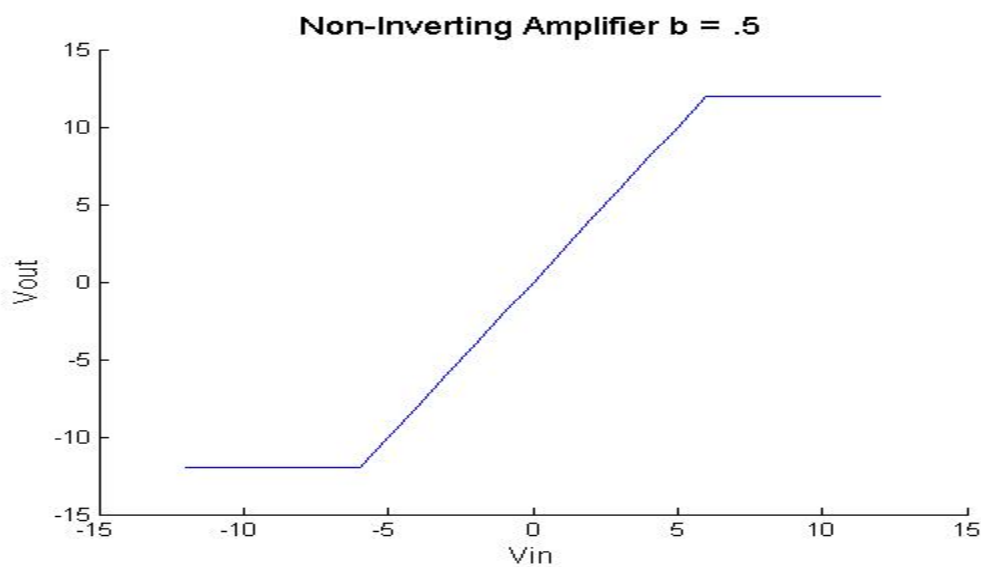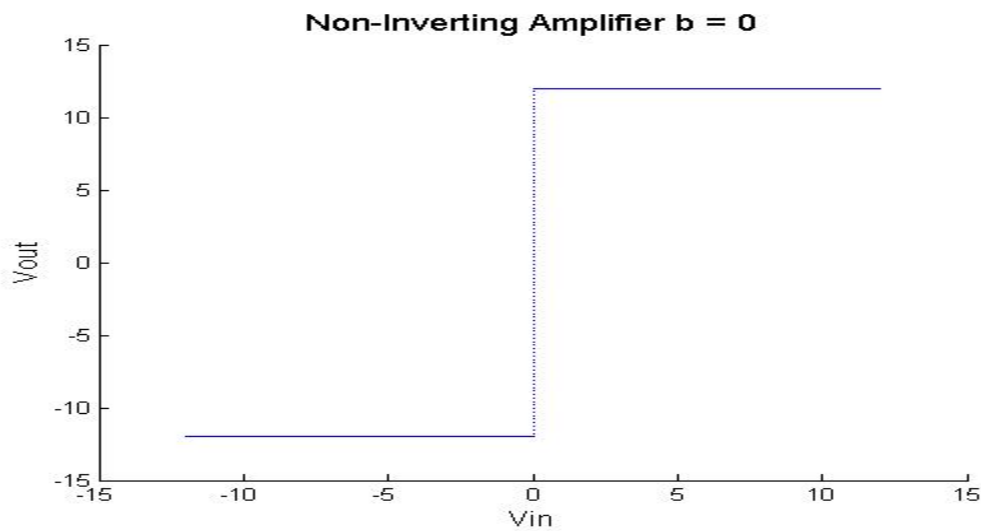III. $V_{in} < b \cdot V_{out}$ and $V_{out} = -V_s$

here are the theoretical graphs for three values of potentiometer b :



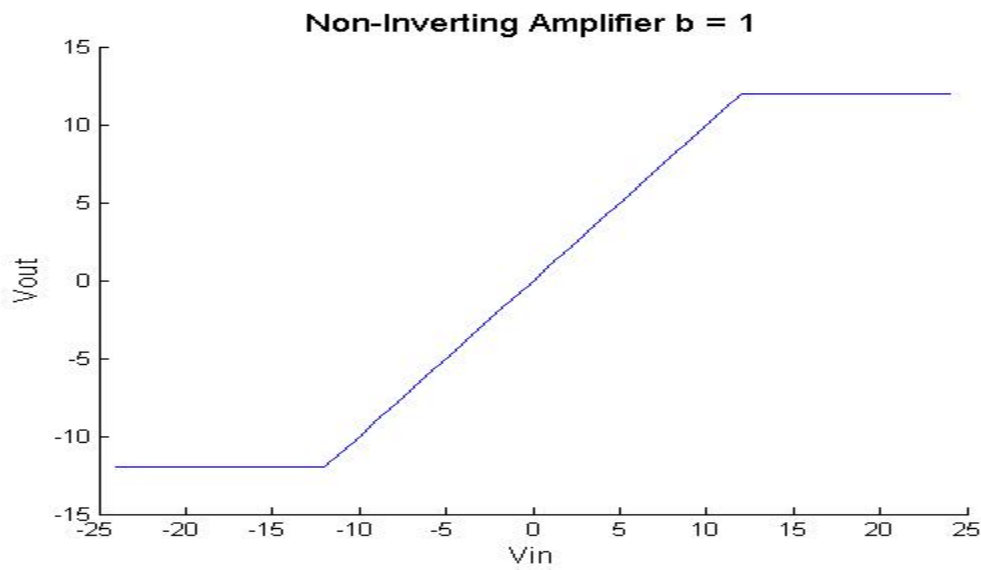

here is the experimental data for three values of pot b ! Any weird noise is probably a result of bad Op-Amp function.

